

# TUTORIAL 4 SOLUTIONS

①

1. Energy stored,  $E = \frac{1}{2}QV$ , where  $Q = \text{charge}$ ,  $V = \text{p.d.}$   
when capacitor is fully  
charged.

Alternatively, we may use  $C = \frac{Q}{V}$  to eliminate either  
 $Q$  or  $V$  and get a different expression for  $E$ .

$$(i) \quad Q = CV \rightarrow E = \frac{1}{2}(CV)V = \frac{1}{2}CV^2,$$

$$(ii) \quad V = \frac{Q}{C} \rightarrow E = \frac{1}{2}Q\left(\frac{Q}{C}\right) = \frac{1}{2}\frac{Q^2}{C}.$$

Here, we have  $V = 12V$  and  $Q = 10\mu C$ .

$$\text{Then, } E = \frac{1}{2}QV = \frac{1}{2} \times 10 \times 10^{-6} \times 12 = 6 \times 10^{-5} \\ = 60 \times 10^{-6} \text{ J}$$

$$\text{i.e. } E = \underline{60\mu\text{J}}.$$

$$2. \quad \left. \begin{array}{l} C = 10\mu\text{F} \\ Q = 20\mu\text{C} \end{array} \right\}$$

$$E = \frac{1}{2}QV = \frac{1}{2}\frac{Q^2}{C}$$

$$= \frac{1}{2} \frac{(20 \times 10^{-6})^2}{10 \times 10^{-6}}$$

$$= \frac{1}{2} \frac{(20)^2 \times 10^{-6} \times 10^{-6}}{10 \times 10^{-6}}$$

$$= \frac{1}{2} \frac{400 \times 10^{-6}}{10}$$

$$\text{i.e. } E = 200 \times 10^{-7} = \underline{20\mu\text{J}}.$$

3.  $C = 100 \mu\text{F}$   
 $V = 100 \text{V}$

$$E = \frac{1}{2} QV = \frac{1}{2} CV^2$$


$$= \frac{1}{2} \times 100 \times 10^{-6} \times (100)^2$$

$$= 50 \times 10^{-6} \times 10^4$$

i.e.  $E = 0.5 \text{ J}$ .

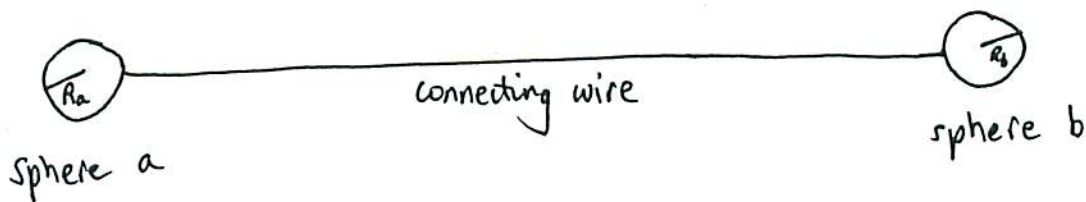4. Capacitance  $C = \frac{Q}{V}$  is the amount of charge stored per unit voltage.

Isolated (i.e. not grounded) conducting sphere has  $C = 4\pi\epsilon R$ ,  
 where, for air,  $\epsilon \approx \epsilon_0 \rightarrow C \approx 4\pi\epsilon_0 R$ , for sphere in air.



Charge will distribute itself until the potential of each sphere is the same.

(a)  $R_a = R_b \Rightarrow C_a = C_b \Rightarrow$  each sphere will have the same charge at the same potential


$\rightarrow 1 \mu\text{C}$  will distribute evenly between the spheres ( $0.5 \mu\text{C}$  each)

(b)  $C_a = \frac{Q_a}{V}$   
 $C_b = \frac{Q_b}{V}$

$$\rightarrow \frac{Q_a}{Q_b} = \frac{C_a}{C_b} = \frac{4\pi\epsilon_0 R_a}{4\pi\epsilon_0 R_b} = \frac{60}{20} = 3, \text{ e.g. } Q_a = 3Q_b$$

and  $Q_a + Q_b = 1 \mu\text{C}$

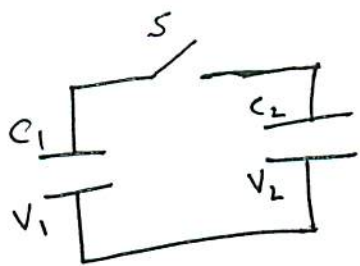Simultaneous equations for  $Q_a$  and  $Q_b$  } Substitute  $3Q_b + Q_b = 1 \mu\text{C}$  i.e.  $4Q_b = 1 \mu\text{C}$   
 i.e.  $Q_b = \frac{1}{4} \mu\text{C}$  and  $Q_a = \frac{3}{4} \mu\text{C}$ .



$$(a) E = \frac{1}{2} C_1 V_1^2$$

$$= \frac{1}{2} \times 10 \times 10^{-6} \times (50)^2$$

$$= \frac{25}{2} \times 10^{-3} = 1.25 \times 10^{-2} \text{ J.}$$

(b) The charge  $Q_1$  on  $C_1$  will be shared between  $C_1$  and  $C_2$  so that the potential difference across each capacitor,  $V_{\text{new}}$ , is the same.

Denoting the capacitance of the parallel combination as  $C_{\text{new}}$ , we will have that  $C_{\text{new}} = \frac{\text{total charge}}{V_{\text{new}}} = \frac{Q_1}{V_{\text{new}}}$ .

→ working out  $Q_1 = C_1 V_1$  and  $C_{\text{new}}$  (from  $C_{\text{new}} = C_1 + C_2$ ) will give  $V_{\text{new}} = \frac{Q_1}{C_{\text{new}}}$ .

Here,  $Q_1 = C_1 V_1 = 10 \times 10^{-6} \times 50 = 5 \times 10^{-4} \text{ C.}$

$$C_{\text{new}} = C_1 + C_2 = (10 + 2.5)_{\mu\text{F}} = 12.5 \times 10^{-6} \text{ F.}$$

$$\rightarrow V_{\text{new}} = \frac{5 \times 10^{-4}}{12.5 \times 10^{-6}} = 40 \text{ V.}$$

(c) Total energy (after connection),  $E = \frac{1}{2} C_1 V_{\text{new}}^2 + \frac{1}{2} C_2 V_{\text{new}}^2 = \frac{1}{2} C_{\text{new}} V_{\text{new}}^2$   
(Can use either to calculate  $E$ )

$$\therefore E = \frac{1}{2} C_{\text{new}} V_{\text{new}}^2 = \frac{1}{2} \times 12.5 \times 10^{-6} \times (40)^2$$

$$\therefore E = 100 \times 10^{-4} = 1.00 \times 10^{-2} \text{ J.}$$


Energy stored before connection was  $1.25 \times 10^{-2} \text{ J} \rightarrow 0.25 \times 10^{-2} \text{ J}$  has been converted to some other form of energy.

→ most of the 'lost energy' will be converted to heat in the circuit.

6. The 'relative permittivity' of a medium,  $\epsilon_r$ , is defined through

(H)

the equation:

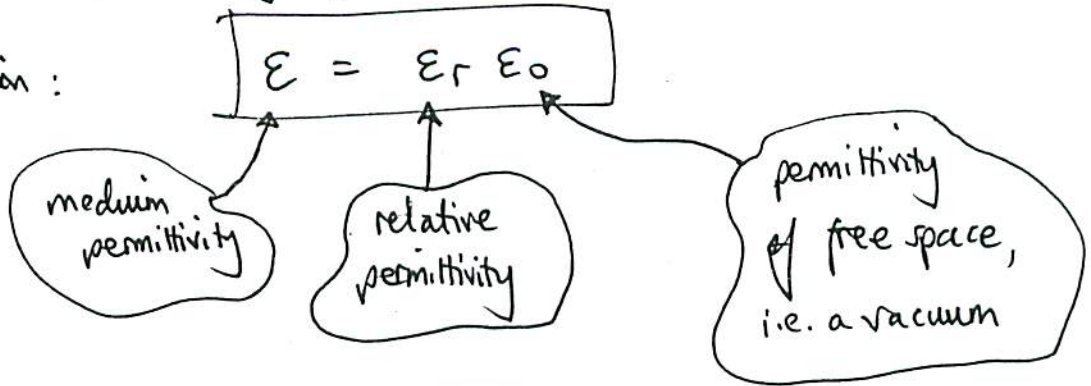



So, we could say that

$$\epsilon_r = \frac{\epsilon}{\epsilon_0}$$

It tells us how much

permittivity a medium has when compared to (expressed as a factor of multiplication)  $\epsilon_0$  i.e. that of a vacuum. By "permittivity", we can describe this as the degree to which a medium "permits" the storage of charge. Note that  $\epsilon_r$  is also called the "dielectric constant".

7.  $V = 400V$

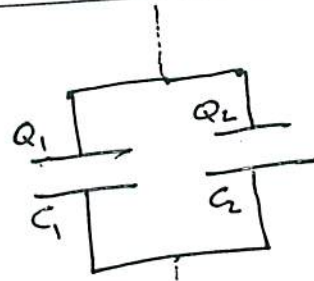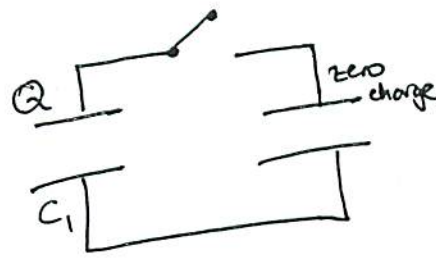

where

$$Q = Q_1 + Q_2 = \text{total charge stored}$$

$V_{\text{new}} = 50V$

(a)

Parallel combination  $\rightarrow C_{\text{new}} = C_1 + C_2$

$$\text{i.e. } C_{\text{new}} = \frac{\epsilon_0 A}{d} + \frac{\epsilon_r \epsilon_0 A}{d}$$

( $\epsilon_r$  for air = 1)

$$\text{i.e. } C_{\text{new}} = \frac{\epsilon_0 A}{d} (1 + \epsilon_r)$$

(note that 'identical dimensions'  $\rightarrow \frac{A}{d}$  same for both)

$$\text{i.e. } C_{\text{new}} = C_1 (1 + \epsilon_r)$$

Also  $C_{\text{new}} = \frac{\text{total charge}}{V_{\text{new}}} = \frac{Q}{50} \quad \therefore Q = 50 C_{\text{new}}$

$\therefore Q = 50 C_1 (1 + \epsilon_r)$

7. (b)  $\epsilon_r = ?$

where  $Q = 50(1 + \epsilon_r) C_1$

(5)

Before connection

$$C_1 = \frac{Q}{V} \quad \text{i.e.} \quad Q = C_1 V$$

$$\therefore \cancel{C_1} V = 50 (1 + \epsilon_r) \cancel{C_1}$$

$$\therefore V = 50 (1 + \epsilon_r) \quad , \quad \text{where } V = 400 \text{ V (given)}$$

$$\therefore \frac{400}{50} = 1 + \epsilon_r$$

$$\therefore 8 = 1 + \epsilon_r \quad \rightarrow \quad \underline{\epsilon_r = 7.}$$

(c) Energy before

$$E = \frac{1}{2} C_1 V^2 = \frac{1}{2} C_1 (400)^2$$

$$E = 80,000 C_1 .$$

Energy after

$$E = \frac{1}{2} C_1 V_{\text{new}}^2 + \frac{1}{2} C_2 V_{\text{new}}^2$$

$$= \frac{1}{2} C_1 V_{\text{new}}^2 + \frac{1}{2} (C_1 \epsilon_r) V_{\text{new}}^2 \quad , \quad \text{since } C_2 = \epsilon_r C_1$$

$$= \frac{1}{2} C_1 (50)^2 + \frac{1}{2} C_1 \cdot 7 \cdot (50)^2$$

$$E = C_1 (10,000) .$$

i.e. energy stored drops from  $80,000 C_1 \rightarrow 10,000 C_1$

$\rightarrow$  usually most of the difference leads to heating of the circuit components.

8. Time constant,  $\tau = RC$

(it is a characteristic time reflecting how long it takes to charge or discharge the capacitor)

Here,  $\tau = 500 \times 10^3 \times 2 \times 10^{-6}$

i.e.  $\tau = 1000 \times 10^{-3} = 1 \text{ s.}$



---

9.  $\tau = RC$ ,  $R = 50 \text{ k}\Omega = 50 \times 10^3 \Omega$   
 $C = 20 \mu\text{F} = 20 \times 10^{-6} \text{ F}$

$\rightarrow \tau = 50 \times 10^3 \times 20 \times 10^{-6} = 1000 \times 10^{-3} = 1 \text{ s.}$

---

10.

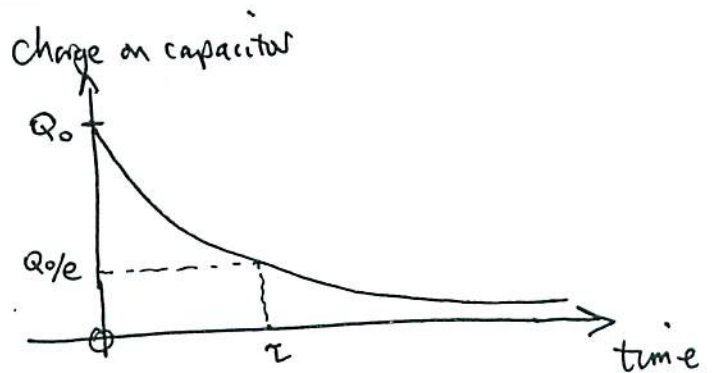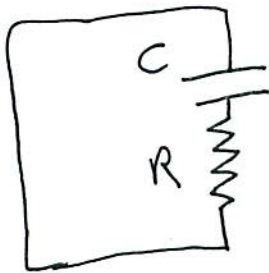

(in fact, after each time period of  $\tau$ , the charge stored decreases by a factor of  $\frac{1}{e}$ )

$\tau = RC$

i.e.  $\tau = 500 \times 10^3 \times 5 \times 10^{-6}$

i.e.  $\tau = 2500 \times 10^{-3}$

i.e.  $\tau = 2.5 \text{ s.}$

---